
# Implementation of DIFFERENT-Gate using VHDL

### OBJECTIVE:

To implement different gate using VHDL and verify its waveform in Xilinx.

### • INTRODUCTION:

### 1. NAND GATE:

 


 $X = \overline{A.B}$ 


| Α | В | X |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

#### Source Code:


```
29
30
   entity OHO is
       Port ( X : in STD LOGIC;
31
               Y : in STD_LOGIC;
32
33
               Z : out STD_LOGIC);
34
    end OHO;
35
36
    architecture Behavioral of OHO is
37
38
    Begin
39
       Process (X, Y)
40
          Begin
             If (X = '1') and Y = '1') then
41
42
                 Z <= '0';
43
             Else
44
                 Z <= '1';
45
          End if:
46
       End process:
47
48
    End Behavioral;
```

# Output:

 

 


# 2. NOR GATE:

 


#### LAB: 2 EMBEDDED SYSTEM

 
#### Source Code:

```
29
30
    entity OHO is
31
       Port ( X : in STD LOGIC;
32
               Y : in STD LOGIC:
33
                Z : out STD LOGIC);
34
    end OHO;
35
36
    architecture Behavioral of OHO is
37
38
   Begin
39
       Process (X, Y)
40
          Begin
             If (X = '0') and Y = '0') then
41
42
                 Z <= '1';
             Else
43
44
                 Z <= 'O';
45
          End if:
46
       End process;
47
48
    End Behavioral;
```



 

## 3. OR GATE:

 


| A | В | gate<br>A+B |  |
|---|---|-------------|--|
| 0 | 0 | 0           |  |
| 0 | 1 | 1           |  |
| 1 | 0 | 1           |  |
| 1 | 1 | 1           |  |

#### Source Code:

```
29
30
    entity OHO is
31
        Port ( X : in STD LOGIC;
32
               Y : in STD LOGIC;
33
               Z : out STD LOGIC);
   end OHO;
34
35
36
   architecture Behavioral of OHO is
37
38 Begin
39
       Process (X, Y)
40
          Begin
             If (X = '0') and Y = '0') then
41
                Z <= '0';
42
43
             Else
                Z <= '1';
44
45
          End if:
46
       End process;
47
   End Behavioral;
48
```


| End Time:<br>1000 ns |   | 50 ns | 150 ns | 250 n | s<br>II | 350 ns | 450 ns | 550 ns | 650 ns |
|----------------------|---|-------|--------|-------|---------|--------|--------|--------|--------|
| <b>™</b> ×           | 1 |       |        |       |         |        |        |        |        |
| <b>∑</b> ∏ Y         | 1 |       |        |       |         |        |        |        |        |
| ₹¶Z                  | 1 |       |        |       |         |        |        |        |        |
|                      |   |       |        |       |         |        |        |        |        |

### 4. **X-OR GATE:**

 

 
#### Source Code:

```
29
30
    entity OHO is
31
        Port ( X : in STD_LOGIC;
32
                Y : in STD LOGIC;
33
                Z : out STD LOGIC);
34
    end OHO;
35
    architecture Behavioral of OHO is
36
37
38
    Begin
39
       Process (X, Y)
40
           Begin
41
              If (X = '1') and Y = '1') then
                 Z <= '0';
42
              Elsif (X = '0') and Y = '0') then
43
                 Z <= '0';
44
45
              Else
46
                 Z <= '1';
47
           End if:
48
       End process:
```



### 5. X-NOR GATE:

 


$$Y = (\overline{A \oplus B}) = (A.B + \overline{A}.\overline{B})$$

| Α | В | Υ |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |
 
#### Source Code:

```
30
    entity OHO is
31
         Port ( X : in STD LOGIC;
32
                Y : in STD_LOGIC;
33
                Z : out STD LOGIC);
34
    end OHO;
35
36
    architecture Behavioral of OHO is
37
38
    Begin
       Process (X, Y)
39
40
           Begin
              If (X = '1') and Y = '1') then
41
42
                 Z <= '1';
43
              Elsif (X = '0') and Y = '0') then
44
                 Z <= '1';
45
              Else
46
                 Z <= '0';
47
           End if:
48
       End process;
```



#### DISCUSSION:

The implementation of the DIFFERENT-Gate using VHDL on the Xilinx platform was successful. After overcoming some initial syntax errors, the VHDL code was corrected, and the gate functioned as expected during simulation. The project helped me better understand VHDL and FPGA design.

**FPGA Design** refers to the process of creating digital circuits and systems using Field-Programmable Gate Arrays (FPGAs). An FPGA is a type of integrated circuit that can be programmed or configured to perform specific tasks. Unlike traditional fixed-function hardware, FPGAs allow designers to program custom logic and functionality.

### CONCLUSION:

The DIFFERENT-Gate was successfully implemented and simulated. This project enhanced my skills in VHDL coding and FPGA design, providing valuable hands-on experience with embedded systems.